Mid Term Question Paper

IE 501; Microprocessor & Microcontrollers; Total Marks: 25

The name and photo associated with your Google account will be recorded when you upload files and submit this form. Not **b16it242@cit.ac.in**? Switch account

* Required

Email address *
b16it242@cit.ac.in
Write your name * DIPANKAR RABHA
Write your roll no * Gau-C-16/242
Your Branch *
○ CSE

Multiple Choice Questions [15-marks] a) Q1 to Q12 has only one correct answer; b) Q13 to Q15 have more than one correct answers; c) There is no negative marking.	
Q1: Which of the following is not a data transfer instruction? *	1 point
MOV A,M	
O LDA 2600H	
O RAL	
○ SPHL	
Other: DAS	
Q2: In the instruction DCR & INR, which of the following flag bit is not	1 point
affected? *	i poiit
○ Zero	
Sign	
Parity	
Carry	


Q3: 8085 enters into a wait state after the recognition of *	1 point
O HOLD	
READY	
RESET	
INTR	
Q4: Which of the following is not an example of 8085 instruction category	? 1 point
O Data transfer	
Arithmetic and Logic	
Branching	
Cache memory transfer	
Q5: In memory mapped I/O, which of the following instructions will not be there? *	1 point
LDA	
○ STA	
○ ADD M	
○ IN	


Q6: Which one of the following instructions may be used for clearing accumulator content? *	1 point
◯ XRA A	
SUB A	
MVI A,00H	
All of these	
Q7: Which of the following instruction requires the highest number of T-states for execution? *	1 point
XTHL	
O CALL	
○ STAX D	
O DAD H	
Q8: Which of the following is not a type of computer language? *	1 point
Medium level language	
High level language	
Cow level language	
All of these	

Q9: The only language which can be understood by the computer is *	1 point
Machine language	
O High level language	
Assembly language	
O None of these	
Q10: (FE35 H) XOR (CB15 H) is equal to *	1 point
O 3320 H	
○ FF35 H	
○ FF50 H	
Q11: The output of a logic gate is "1" when all of its input is at logic "0". Then the gate is either *	1 point
A NAND or an EX-OR gate	
A NOR or an EX-NOR gate	
An OR or an EX-NOR gate	
An AND or an EX-OR gate	

Q12: For how many T-states ALE will be high during a machine cycle? *	1 point
1 T-state	
2 T-state	
3 T-state	
4 T-state	
Q13: Which of the following instruction's opcode fetch consists of 6-T states? *	1 point
☐ STA	
✓ CALL	
PUSH	
LDA	
Q14: Which of the following instruction's size is 2-byte? *	1 point
ANI ANI	
ADI	
☐ ADD M	
☐ ADD C	

Q15: In memory mapped I/O, the instruction(s) used to transfer the data of accumulator is/are: *	1 point
☐ IN instruction	
STA instruction	
✓ LDA instruction	
All of these	
Short type questions [10-marks] Write the answers in paper and attach the scan copy in pdf or image format	
Q16: State the need to demultiplex the bus ADO-AD7. How is demultiplexing done? 1. Add file	? points
Q17: The memory address of the last location of an 16kB memory chip is 2 FFFF H. Find the starting address. 1. Add file	? points

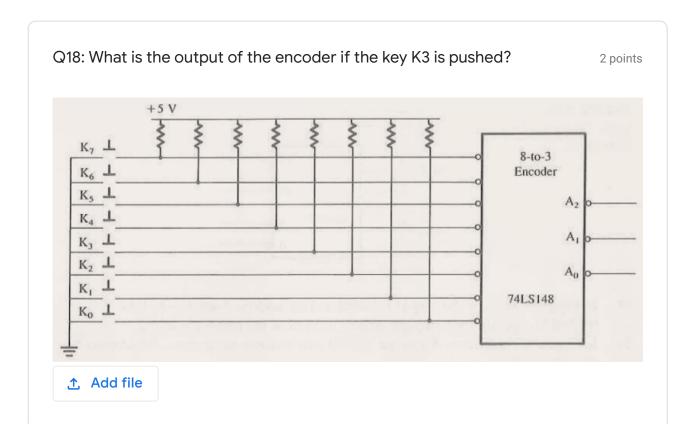

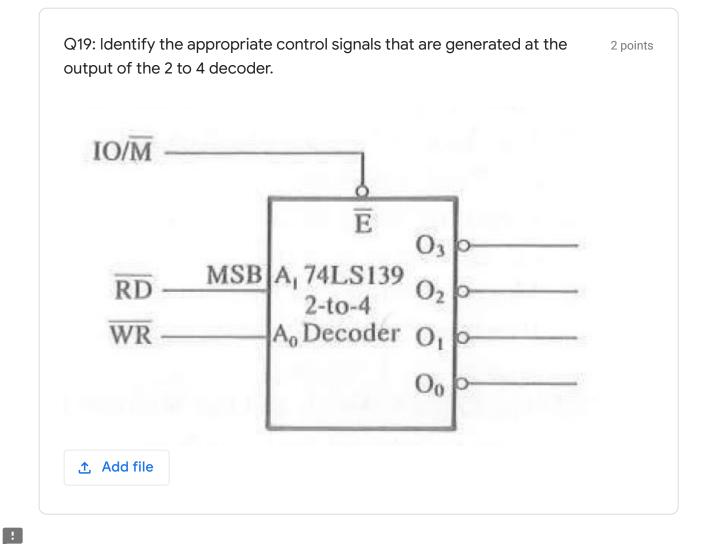

Q20: In the following figure, exchange the address lines A12 and A14, and identify the memory map. A₁₄ A₁₅ $\frac{\overline{RD}}{\overline{WR}}$ IO/M - \overline{E}_2 \overline{E}_3 CE OE WE 3-to-8 6116 Decoder 74LS138 O₁ R/W Memory MSEL, 2048×8 O_0 Data Lines

Submit

Never submit passwords through Google Forms.

This form was created inside of Central institute of Technology Kokrajhar. Report Abuse

Google Forms